Roll No.

Total Pages : 3

РМСА/М-20 10621

COMPUTER ORGANIZATION & NETWORKING FUNDAMENTALS

Paper-CS-DE-11

Time Allowed : 3 Hours] [Maximum Marks : 80

Note : Attempt five questions in all, selecting at leastone question from each Unit. Question No. 1 iscompulsory. All questions carry equal marks.

Compulsory Question

1. Answer the following questions in brief : $4 \times 4 = 16$

- (i) Distinguish between Hardware and Software.
- (ii) What are rules to draw a truth table?
- (iii) What is T-type flip-flop? Write its excitation table.
- (iv) Explain about Telnet.

UNIT-I

 (i) Explain the following about Hard Disk : track, sector, cylinder, latency time, seek time, access time.

10621/K/396

P. T. O.

- (ii) Convert (39.75)₁₀ into octal and hexadecimal number systems.
 8
- 3. (i) What are BCD codes? Represent (947)₁₀ in 2421, excess-3 and cyclic BCD codes. 8
 - (ii) Perform (-13)₁₀+(-19)₁₀ in 1's complement and 2's complement form considering register size 8 bit.

UNIT-II

- 4. (i) What are cononical representation of Boolean function? Explain with an example. 8
 - (ii) Simplify the following Boolen function using K-map : $F(A,B,C,D)=\Sigma(0,1,2,8,10,11,14,15)$. 8
- 5. (i) What is full adder? Design it using two half adders, one AND gate and one OR gate. 8
 - (ii) Design a BCD code converter to convert 8421into excess-3 BCD code.

UNIT-III

6. (i) What is JK flip-flop? Explain its working with its logic diagram. Also construct its excitation table.
 8

10621/K/396

2

- (ii) What is RK flip-flop? How can you convert it into D-type flip-flop? Explain.
- 7. (i) What is register? Design a 4-bit register with parallel load using D flip-flops. 8
 - (ii) What is counter? Design a 4-bit binary ripple counter and explain its working.

UNIT-IV

- 8. (i) Explain the following : repeater, network interface card (NIC), bridge and router. 8
 - (ii) What are wired transmission media? Explain them in brief.
- 9. (i) What are internet services? Explain FTP service. 8
 - (ii) Explain the following : search engine, DSL service.

3